 


## EE3230 VLSI Design HW #2


110061217 王彦智

1. Please design an inverter using a NMOS and a resistor.
  - a.  $4680.25\Omega$ , when  $V_{in}$  is 900mv,  $V_{out}$  is 900.00mv.



X axis:  $V_{in}(v)$ -Y axis:  $V_{out}(v)$

 - b.  $V_{out} = 148.12\text{mV}$ ,  $I = 254\mu\text{A}$  and NMOS is operating in triode region.




Blue line: X axis:  $V_{in}(v)$ -Y axis: current flow through inverter( $I$ )

Red line: X axis:  $V_{in}(v)$ -Y axis:  $V_{out}(v)$

- c. Shift left, why?

c.

 

if  $V_m = 0.9$


$$\rightarrow V_{out} = 1.8 - R_d \left( \frac{1}{2} \times \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2 \right)$$

when  $R_d$  is larger, and other variable are fixed

$V_{out} \downarrow$ , when  $R_d \uparrow$

$\Rightarrow V_m$  on transition point  $\downarrow$ , when  $R_d \uparrow$

 
so the transition point shift left when  $R_d$  is larger.



X axis:  $V_{in}(v)$ -Y axis:  $V_{out}(v)$

Red line when  $r=6480.25$ ; Green line: when  $r = 2*6480.25$

d.  $V_{in0} = 749.91mV$

 

X axis:  $V_{in}(v)$ -Y axis:  $V_{out}(v)$

e. Find  $V_{il}$ ,  $V_{oh}$ ,  $V_{ih}$  and  $V_{ol}$

$R(\Omega)$	$V_{il}(mV)$	$V_{oh}(mV)$	$V_{ih}(mV)$	$V_{ol}(mV)$
6480.25	532.13	1726.43	1163.57	339.92
12960.50	478.21	1739.25	966.44	229.56

f. Noise margin

$R(\Omega)$	NML(mV)	NMH(mV)
6480.25	192.21	562.86
12960.50	248.65	772.81

2. CMOS 3-input NAND gate

a. Ratio

Gate	NMOS(W/L)	PMOS(W/L)	NMOS/PMOS
NAND	$1.2u/0.2u = 6.00$	$0.486u/0.2u = 2.43$	$6/2.43 = 2.46$
Inverter	$1.2u/0.2u = 6.00$	$4.23u/0.2u = 21.15$	$6/21.15 = 0.28$
Inverter(模範生)	$0.4u/0.2u = 2.00$	$1.81u/0.2u = 9.05$	$2/9.05 = 0.22$

2- (a) NAND

Inverter ① Inverter ②

we inverter pmos size same as NAND

$$\frac{\text{ratio of NAND}}{\text{ratio of Inverter}} = \frac{2.46}{0.28} \approx 8.78 \approx 9$$

推測 mobility ratio  $\frac{\mu_n}{\mu_p} = \frac{21.15}{6} \approx 3.5$

2 use 模範生 inverter:

$$\frac{\text{ratio of NAND}}{\text{ratio of Inverter}} = \frac{2.46}{0.22} \approx 11.18$$

推測 mobility ratio  $\frac{\mu_n}{\mu_p} = \frac{9.05}{2} = 4.5$

$\Rightarrow$  假設  $\frac{\mu_n}{\mu_p} = 3$

then for inverter  $\frac{NMOS}{PMOS} = \frac{1}{3}$


NAND input together  $\frac{NMOS}{PMOS} = \frac{3}{1}$

$$\therefore \frac{\text{ratio of NAND}}{\text{ratio of inverter}} = \frac{3/1}{1/3} = 9$$

really close to 1!

誤差不小原因: 未考慮寄生電容、電阻

b. DC voltage transfer

 


X axis: Vin(v)-Y axis: Vout(v)

c. Find  $V_{il}$ ,  $V_{oh}$ ,  $V_{ih}$  and  $V_{ol}$

NAND	$V_{il}(mV)$	$V_{oh}(mV)$	$V_{ih}(mV)$	$V_{ol}(mV)$
Three input	771.05	1692.63	1023.15	96.52

NAND	NML(mv)	NMH(mv)
Three input	674.53	669.48

d. DC voltage transfer

 


X axis: Vin(v)-Y axis: Vout(v)

e. Find Vil, Voh, Vih and Vol

NAND	Vil(mV)	Voh(mV)	Vih(mV)	Vol(mV)
VinC	515.23	1733.41	778.30	101.46

NAND	NML(mv)	NMH(mV)
VinC	413.77	955.11

f. DC voltage transfer

 

X axis: Vin(v)-Y axis: Vout(v)

g. Find Vil, Voh, Vih and Vol

NAND	Vil(mV)	Voh(mV)	Vih(mV)	Vol(mV)
VinA	520.81	1740.62	754.87	109.12

NAND	NML(mv)	NMH(mV)
VinA	411.69	985.75

h. Explain

NAND	Vil(mV)	Voh(mV)	Vih(mV)	Vol(mV)
Three input	771.05	1692.63	1023.15	96.52
VinC	515.23	1733.41	778.30	101.46
VinA	520.81	1740.62	754.87	109.12

NAND	NML(mv)	NMH(mv)
Three input	674.53	669.48
VinC	413.77	955.11
VinA	411.69	985.75

Effective beta ratio of tree different operation: Three input  $> V_{inC} \geq V_{inA}$


When the effective beta ratio of the NAND3 gate will be lower,  $V_{out}$  will falls earlier, transition point will shift left, NML will decrease and NMH will increase.

3. Simulate NAND gate with  $C_{load}$  of 20fF

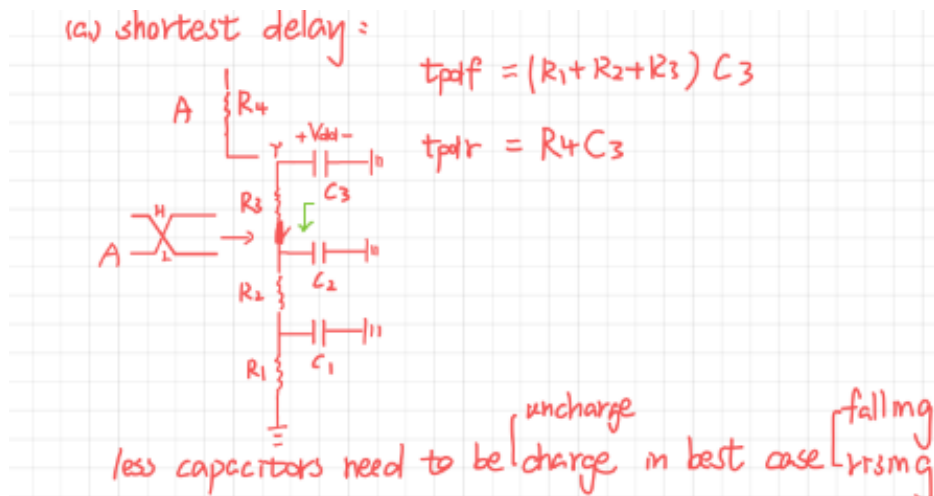a. Explain shortest delay

Rising: switch C from 1 to 0, hold A and B at 1


Falling: switch C from 0 to 1, hold A and B at 1



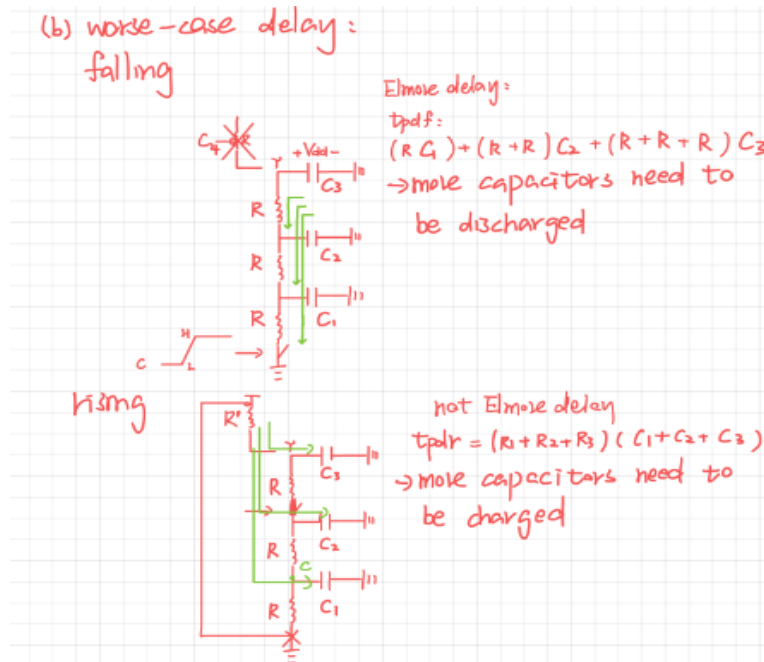b. Explain worse case propagation delays

Rising: switch A from 1 to 0, hold B and C at 1

Falling: switch A from 0 to 1, hold B and C at 1



- c. 5corner
- d. sp netlist

Process	Temperature	tcdr(ps)	tcdf(ps)	tpdr(ps)	tpdf(ps)
TT	25	241.81	80.93	326.21	100.31
FF	-40	192.82	61.08	255.82	72.49
SS	125	517.73	209.90	751.85	283.71
SF	25	214.01	161.21	299.36	213.20
FS	25	441.82	69.26	603.81	84.11

#### 4. M factors of NAND gate

##### a. Propagation delay

tpdf: 102.21ps


tpdr: 102.35ps

tpd = (102.21 + 102.35) / 2 = 102.28ps
 
##### b. m value

When  $m < 25$ : Increasing the size of all transistors, which will let NAND3 gate is able to drive the load capacitance more easily, and the gate capacitance doesn't increase a lot at this point, so the delay is shorter.

When  $m > 25$ : The gate capacitance will be too large as we increase  $m$ . Although driving capability increases, the parasitic delay which is affected by the gate capacitance overweighs the increase of driving capability.



Redline: X axis: m value-Y axis: tpdf(s)

Blueline: X axis: m value-Y axis: tpdr(r)